

# Homework 2 Solution

## Problem 1 (2 marks)

Find the complement of the following function:

$$X + Y(Z + (X + Z)')$$

Change every variable to its complement and exchange ands and ors.

$$\begin{aligned} F' &= X' (Y' + (Z' (X + Z))) \\ &= X' (Y' + (Z'X + Z'Z)) \\ &= X' (Y' + XZ') \end{aligned}$$

Or applying De-Morgan theorem multiple times.

$$\begin{aligned} F' &= X'(Y(Z + (X + Z)'))' \\ &= X' (Y' + (Z + (X + Z)'))' \\ &= X' (Y' + (Z' (X + Z)'))' \\ &= X' (Y' + (Z' (X + Z)')) \\ &= X' (Y' + (Z' (X + Z))) \\ &= X' (Y' + (Z'X + Z'Z)) \\ &= X' (Y' + XZ') \end{aligned}$$

## Problem 2 (5 marks)

For the Boolean Function F, as given in the following truth table:


X	Y	Z	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

- List its minterms  
 $F = \Sigma m(0, 1, 3, 5, 7)$
- List its maxterms  
 $F = \Pi M(2, 4, 6)$
- List the minterms of  $F'$   
 $F' = \Sigma m(2, 4, 6)$
- Express F in sum-of-minterms algebraic form  
 $F = X'Y'Z' + X'Y'Z + X'YZ + XY'Z + XYZ$
- Express F in product-of-maxterms algebraic form  
 $F = (X + Y' + Z) \cdot (X' + Y + Z) \cdot (X' + Y' + Z)$

**Problem 3** (2 marks)

Draw the logic diagram for the following Boolean expression. The diagram should correspond exactly to the equation. Assume the complements of the inputs are not available.


$$B(A'C' + AC) + D'(A + B'C)$$

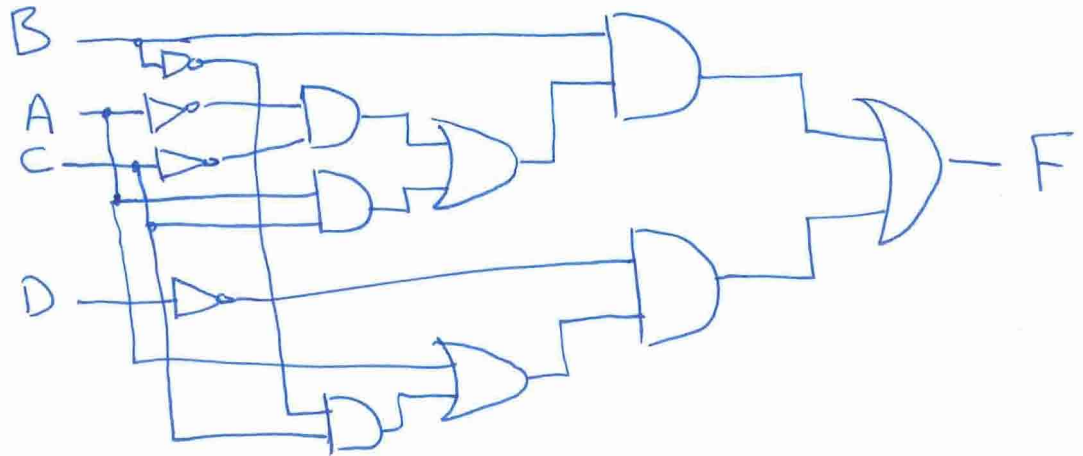


**Problem 4** (6 marks)

Optimize the following Boolean functions by means of Karnaugh map:

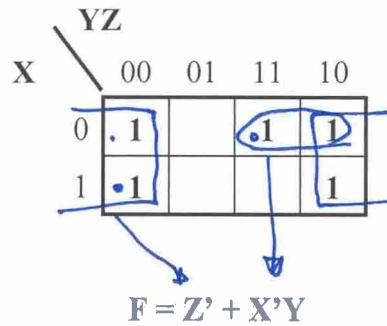
(a)  $F(X, Y, Z) = \Sigma m(0, 2, 3, 4, 6)$



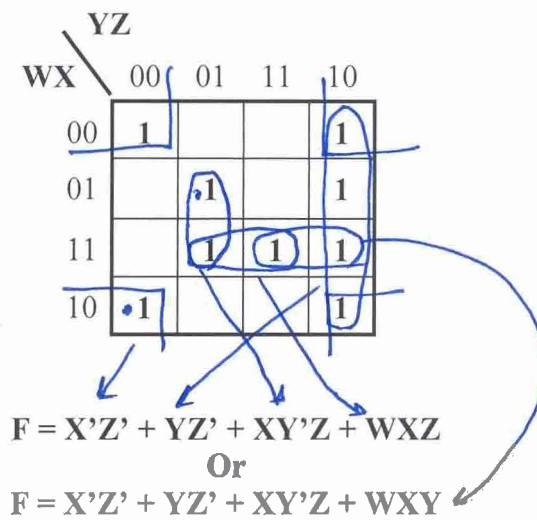(b)  $F(W, X, Y, Z) = \Sigma m(0, 2, 5, 6, 8, 10, 13, 14, 15)$






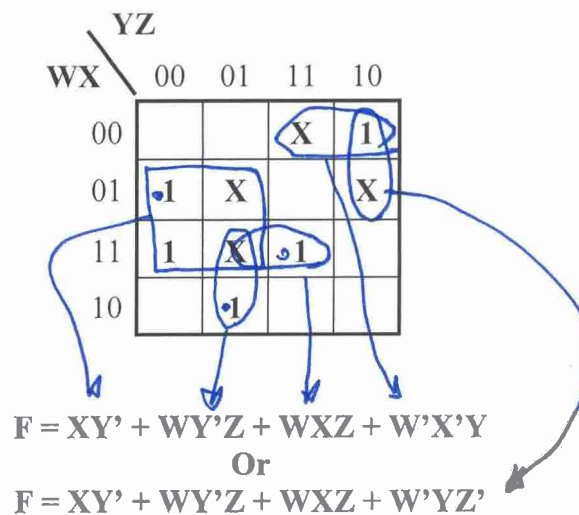(c)  $F(W, X, Y, Z) = \Sigma m(2, 4, 9, 12, 15)$ , with the don't-care conditions  $d(W, X, Y, Z) = \Sigma m(3, 5, 6, 13)$



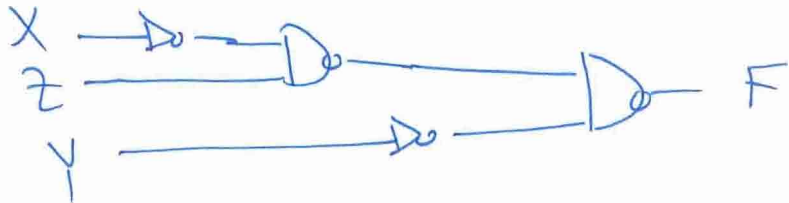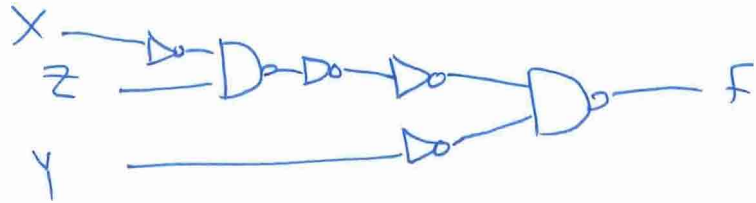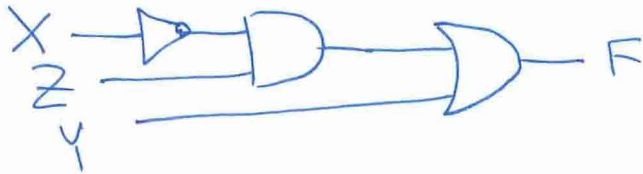**Problem 5** (2 marks)


Implement the following Boolean function using NAND gates only:  $F(X, Y, Z) = X'Z + Y$



$$\overline{\overline{XZ} \cdot \overline{Y}} = \overline{XZ} + Y$$

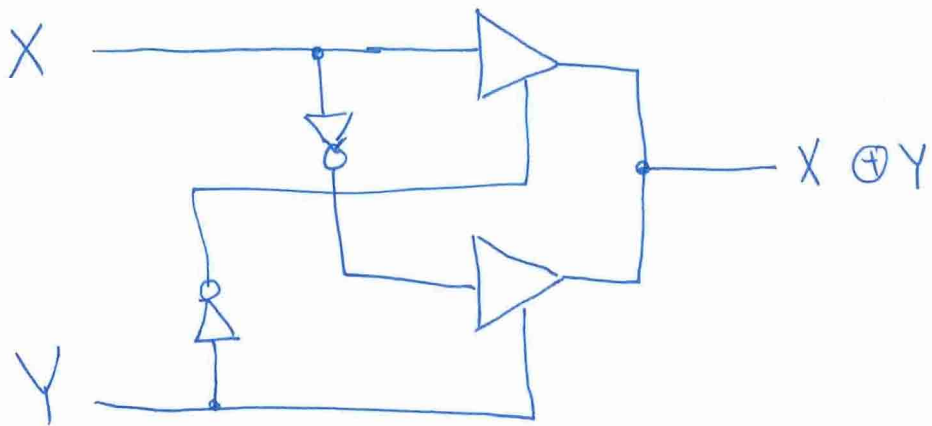**Problem 6** (2 marks)

Construct an exclusive-OR gate by interconnecting two three-state buffers and two inverters.



**Problem 7** (6 marks)

Obtain the truth table of the following functions, and express each function in sum-of-minterms and product-of-maxterms form:

(a)  $(AB + C)(B + AC)$

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$$F = \Sigma m(3, 5, 6, 7)$$

$$F = \Pi M(0, 1, 2, 4)$$

(b)  $ABC' + ABD' + ABD + CD'$

A	B	C	D	F
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

$$F = \Sigma m(2, 6, 10, 12, 13, 14, 15)$$

$$F = \Pi M(0, 1, 3, 4, 5, 7, 8, 9, 11)$$

**Problem 8** (4 marks)(a) Convert the following Boolean expression into SOP then into SOM:  $X' + X(X+Y')(Y+Z')$ 

$$\begin{aligned}
 F &= X' + X(X+Y')(Y+Z') \\
 &= X' + (XX+XY')(Y+Z') \\
 &= X' + (X+XY')(Y+Z') \\
 &= X' + (X)(Y+Z') \\
 &= X' + XY + XZ' \qquad \qquad \qquad (SOP \text{ form})
 \end{aligned}$$

$$\begin{aligned}
 &= X'(Y'Z'+Y'Z+YZ'+YZ) + XY(Z'+Z) + XZ'(Y'+Y) \quad \text{Adding missing minterms} \\
 &= X'Y'Z'+Z'Y'Z+ZYZ'+X'YZ + XYZ'+XYZ + XY'Z'+XYZ' \\
 &= X'Y'Z'+Z'Y'Z+ZYZ'+X'YZ + XYZ'+XYZ + XY'Z' \quad \text{Removing duplicates} \\
 &= X'Y'Z'+Z'Y'Z+ZYZ'+X'YZ + XY'Z' + XYZ'+XYZ \quad (SOM \text{ form})
 \end{aligned}$$

(b) Convert the following Boolean expression into POS then into POM:  $(AB+C)(B+AC')$ 

$$\begin{aligned}
 F &= (AB+C)(B+AC') \\
 &= (A+C)(B+C) (B+A)(B+C') \\
 &= (A+C) (B+C) (A+B) (B+C') \qquad \qquad \qquad (POS \text{ form})
 \end{aligned}$$

$$\begin{aligned}
 & \qquad \qquad \qquad \text{Adding missing maxterms} \\
 &= (A+B'+C)(A+B+C) (A'+B+C)(A+B+C) (A+B+C')(A+B+C) (A'+B+C')(A'+B+C') \\
 & \qquad \qquad \qquad \text{Removing duplicates} \\
 &= (A+B'+C)(A+B+C) (A'+B+C) (A+B+C') (A'+B+C') \\
 & \qquad \qquad \qquad \text{Rearranging} \\
 &= (A+B+C) (A+B+C') (A+B'+C) (A'+B+C) (A'+B+C') \qquad \qquad \qquad (POM \text{ form})
 \end{aligned}$$