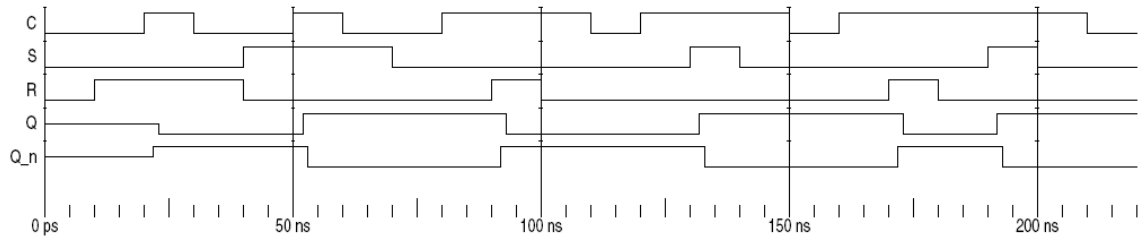



Homework 3 Solution

5-2.




<2 marks>

5-4.

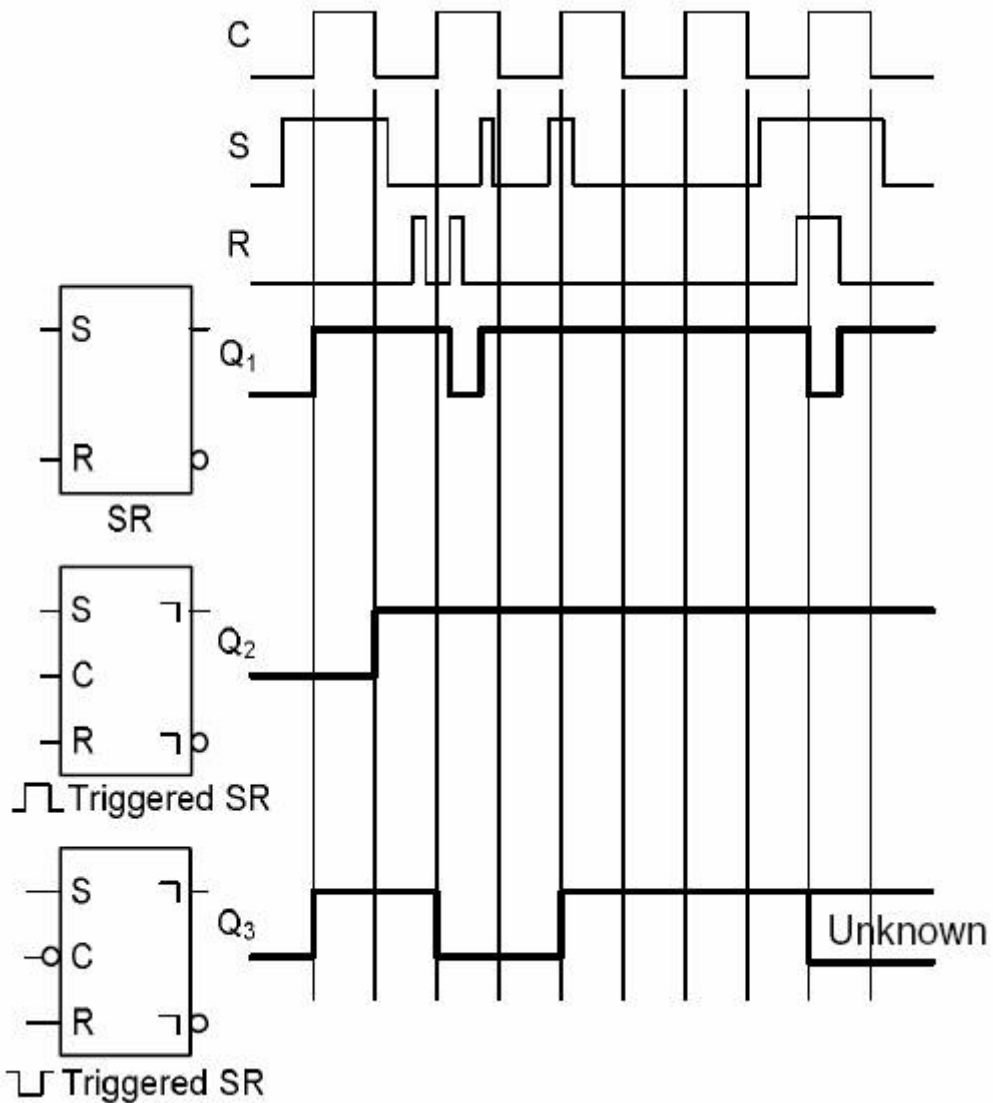


<3 marks>

5-5.

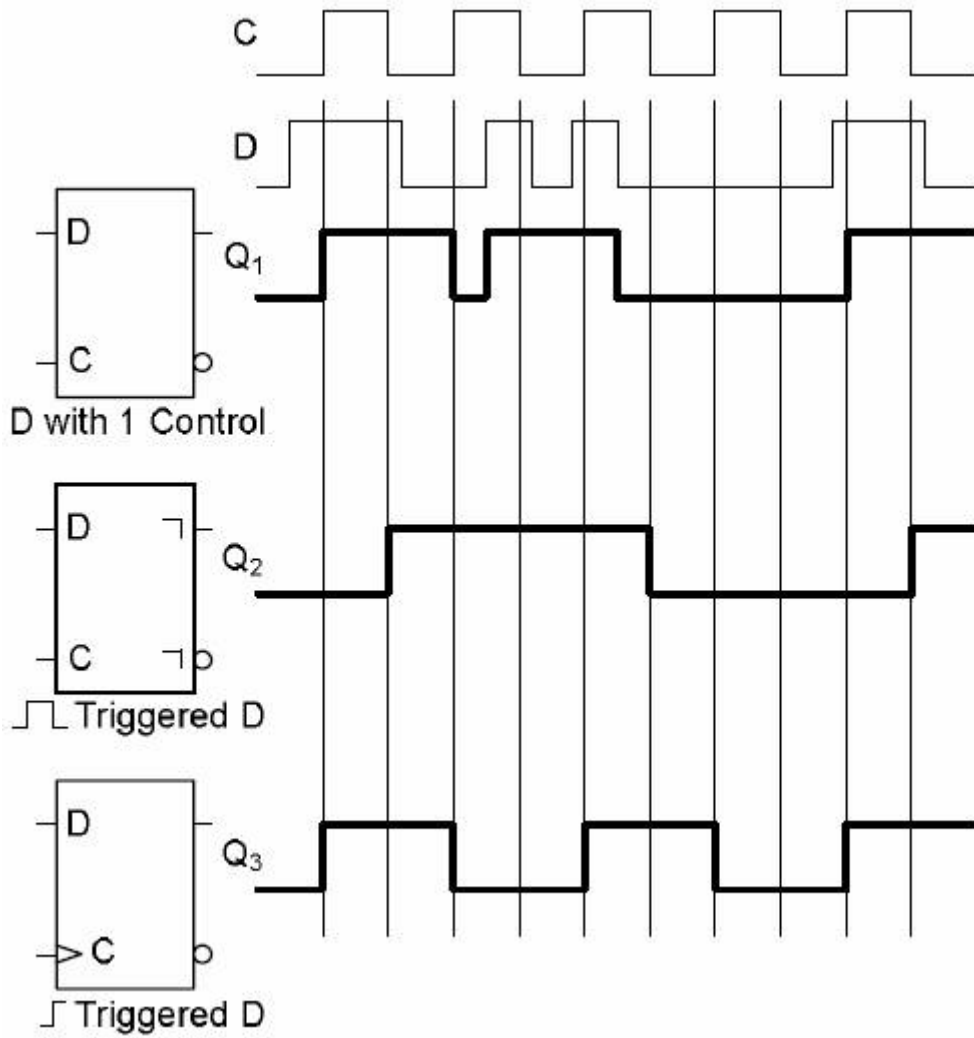


<3 marks>

5-6.

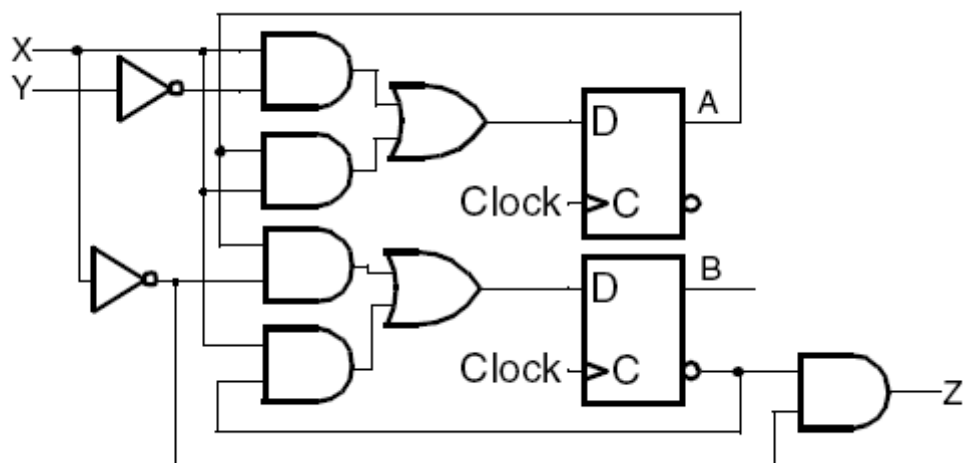

Present State		Inputs		Next State		Output
A	B	X	Y	A	B	Z
0	0	0	0	0	0	1
0	0	0	1	0	0	1
0	0	1	0	1	1	0
0	0	1	1	0	1	0
0	1	0	0	0	0	0
0	1	0	1	0	0	0
0	1	1	0	1	0	0
0	1	1	1	0	0	0
1	0	0	0	0	1	1
1	0	0	1	0	1	1
1	0	1	0	1	1	0
1	0	1	1	1	1	0
1	1	0	0	0	1	0
1	1	0	1	0	1	0
1	1	1	0	1	0	0
1	1	1	1	1	0	0

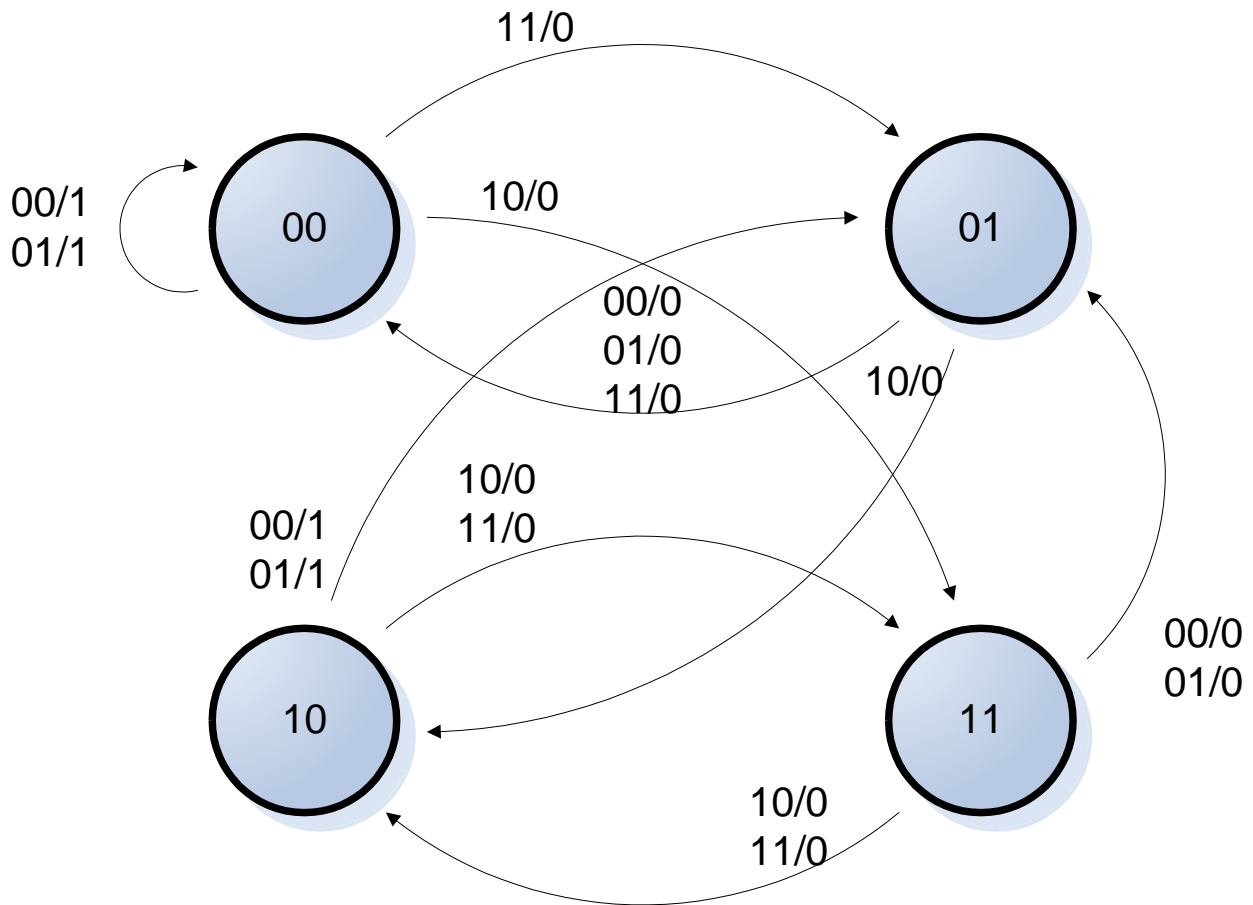


<3 marks>

5-9.

Present State	00	00	01	00	01	11	00	00	01	11	00
Input	0	1	0	1	1	0	0	1	1	0	1
Output	0	0	1	0	0	1	0	0	0	1	0
Next State	00	01	00	01	11	00	00	01	11	00	01

<2 marks>

5-10.

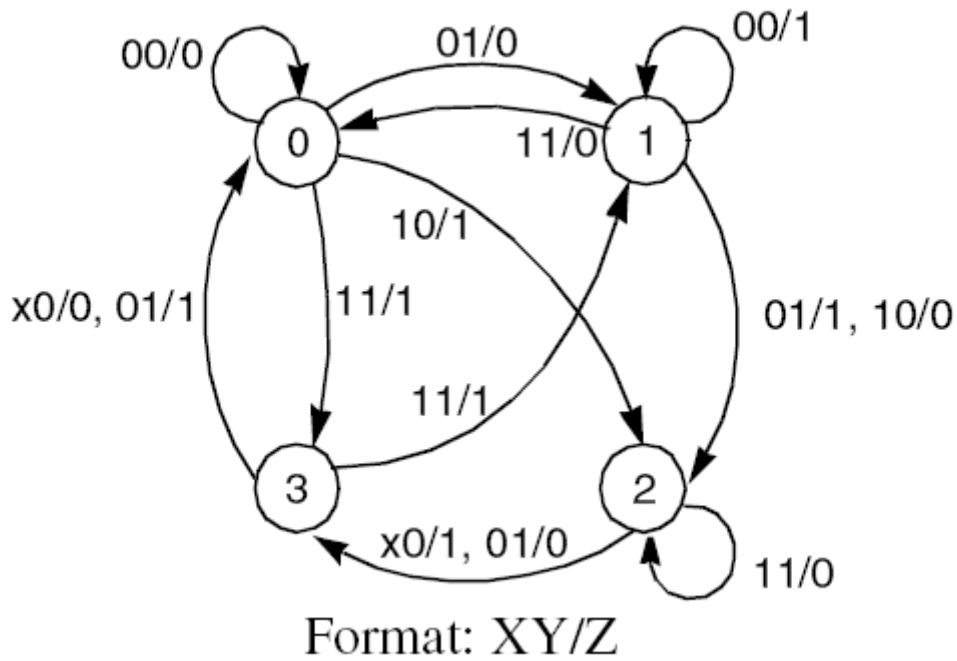


<2 marks>

5-11.

$$S_A = B \quad S_B = \overline{X \oplus A}$$

$$R_A = \overline{B} \quad R_B = X \oplus A$$


Present state		Input	Next state		Output
A	B	X	A	B	Y
0	0	0	0	1	0
0	0	1	0	0	1
0	1	0	1	1	1
0	1	1	1	0	0
1	0	0	0	0	1
1	0	1	0	1	0
1	1	0	1	0	0
1	1	1	1	1	1

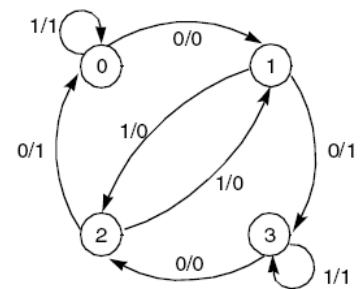


<2 marks>

5-13.

Present State		Input	Next State	
A	B	X	A	B
0	0	0	1	0
0	0	1	0	0
0	1	0	1	1
0	1	1	0	1
1	0	0	0	1
1	0	1	1	0
1	1	0	0	0
1	1	1	1	1

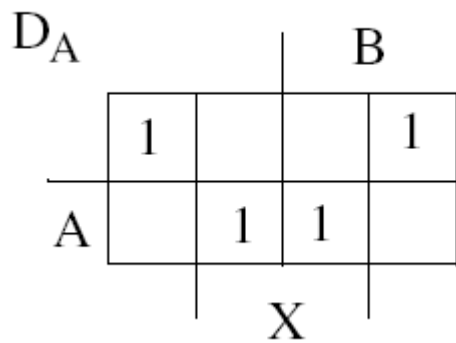

$$D_A = A'X' + AX$$

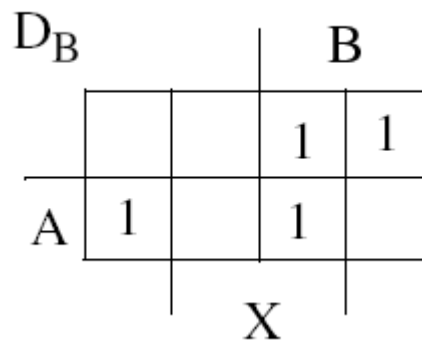

$$D_B = A'B + BX + AB'X'$$

<3 marks>

5-14.

There can be many alternatives for state assignment using 3-bit codes; one alternative is:

State	Code
A	000
B	001
C	010
D	100

The resulting state table is:

Present State	Input		Next State	Output
	X ₁	X ₂		Z
A 000	0	0	A 000	0
A 000	0	1	B 001	0
A 000	1	0	B 001	1
A 000	1	1	A 000	0
B 001	0	0	A 000	0
B 001	0	1	A 000	0
B 001	1	0	D 100	1
B 001	1	1	D 100	1
C 010	0	0	A 000	1
C 010	0	1	A 000	0
C 010	1	0	C 010	1
C 010	1	1	C 010	0
D 100	0	0	C 010	1
D 100	0	1	B 001	1
D 100	1	0	B 001	0
D 100	1	1	C 010	1

<2marks>